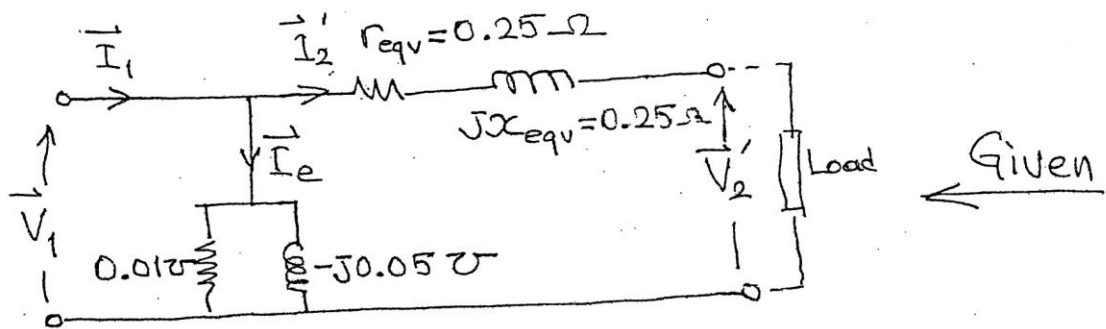


SOLVED PROBLEMS II

✓ Example A 10-kVA, 220/110V, 50-Hz single-phase transformer delivers rated power (operates at full-load) to its load at rated secondary voltage and 0.8 pf lagging. Compute

- Primary voltage (use approximate equivalent circuit),
- Efficiency,
- Voltage regulation.



Soln


Voltage and current phasors should be expressed as complex numbers on complex plane.

Rectangular Form : $\vec{Z} = x + jy$


Polar or Steinmetz Form : $\vec{Z} = r \angle \theta$

Trigonometric Form : $\vec{Z} = r(\cos \theta + j \sin \theta)$

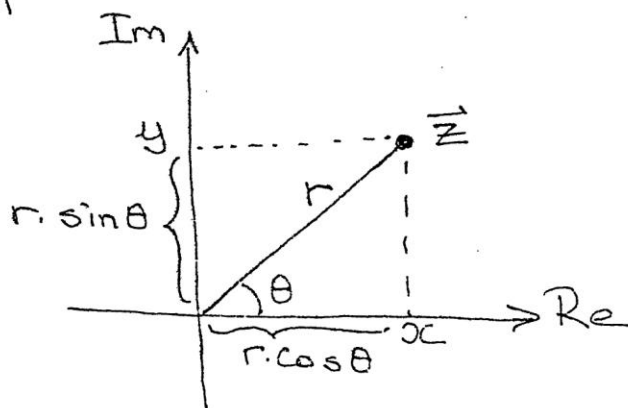Exponential Form : $\vec{Z} = r e^{j\theta}$




a)

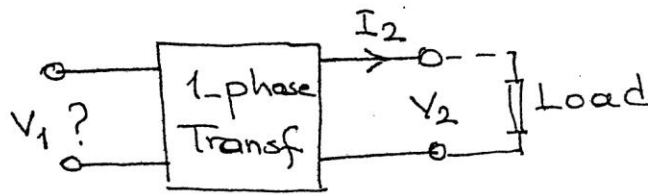

Rated power, $S_{\text{rated}} = S_{\text{out}} = S_{\text{load}} = 10000 \text{ VA}$
delivered to load

At rated secondary, $V_2 = V_{2\text{rated}} = V_{\text{load}} = 110 \text{ V}$
Voltage

At 0.8 pf lagging,

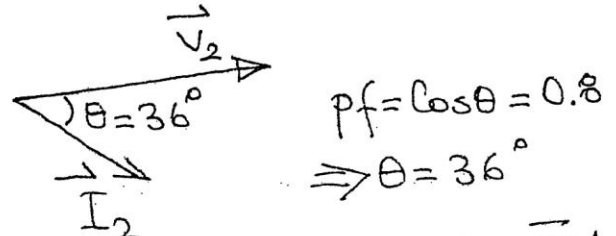

Secondary current, $I_2 = I_{\text{load}} = \frac{S_{\text{out}}}{V_2} = \frac{10000}{110} = 90.90 \text{ A}$

Since equivalent circ is given on the primary side, secondary voltage and current should be referred to primary side.

$V_2' = n \cdot V_2 = 2 \cdot 110 = 220 \text{ V}$ where, $n = (220/110) = 2$

$I_2' = I_2 / n = 90.90 / 2 = 45.45 \text{ A}$


\vec{V}_2' can be chosen as the reference phasor!

Kirchhoff's Voltage Law:

$$\vec{V}_1 = \vec{V}_2' + (r_{\text{eqv}} + jx_{\text{eqv}}) \vec{I}_2'$$

$$\begin{aligned} \vec{V}_1 &= 220 + (0.25 + j0.25) 45.45 (0.8 - j0.6) \\ &= 220 + 45.45 (0.35 + j0.05) \\ &= 235.90 + j2.27 \end{aligned}$$
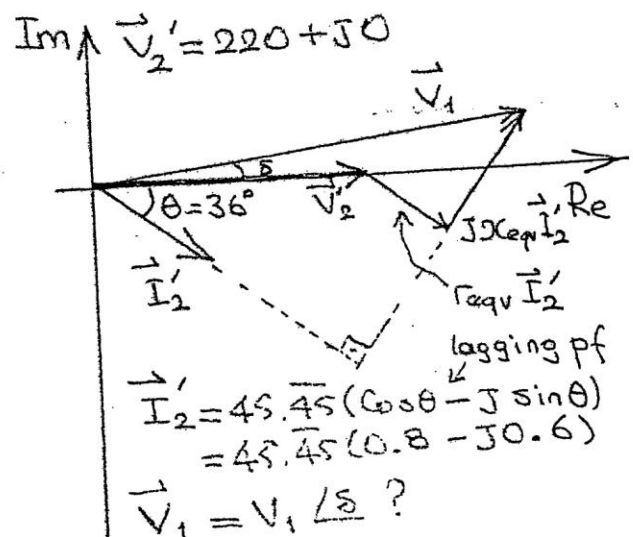
$$\vec{V}_1 = 236 \angle +0.6^\circ \text{ Volts rms //$$



$$b) \text{ Efficiency} = \frac{\text{Output Power}}{\text{Output Power} + \text{Losses}}$$

$$\text{Output Power, } P_{\text{out}} = P_{\text{load}} = S_{\text{out}} \cdot \cos \theta = 10 \text{ kVA} \cdot 0.8 = 8 \text{ kW}$$

$$\text{Copper Loss, } I_2'^2 \cdot r_{\text{eqv}} = (45.45)^2 \cdot 0.25 = 516.5 \text{ W}$$

$$\text{Core loss, } E_1^2 g_c \approx V_1^2 g_c = (236)^2 \cdot 0.01 = 557 \text{ W}$$

$$\therefore \text{ Efficiency, } \eta = \frac{8000}{8000 + 557 + 516.5} = 0.88$$

$$\eta = 88 \% //$$

c) In this problem, voltage regulation is the change in secondary terminal voltage from no-load to full-load:

$$\text{No-load voltage, } V_2' = V_1 = 236 \text{ Volts rms (since } I_2' = 0 \text{ at no-load)}$$


$$\text{Full-load voltage, } V_2' = V_{2\text{rated}} = 220 \text{ V rms}$$

It is usually expressed as a percentage of no-load value:

$$\text{Voltage Regulation} = \frac{236 - 220}{236} \times 100 = +6.8 \% //$$

↑
Drooping terminal voltage characteristic because of the inductive character of the load.

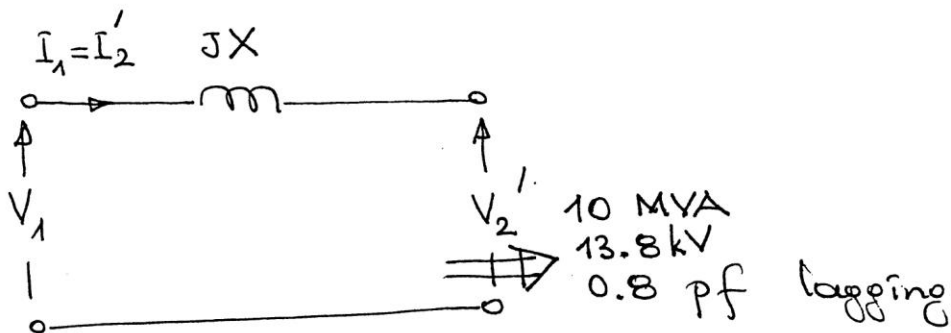Ex A 10 MVA 13.8/79.7 kV step-up transformer has a total leakage reactance of $X = 1.9 \Omega$ referred to primary. Neglecting all transformer losses and magnetizing current, find the primary voltage when transformer is supplying the rated MVA at rated voltage and 0.8 pf lagging.




$$P_{out} = V_2' I_2' \cos \theta$$

$$S_2 = V_2 I_2 = V_2' I_2' = 10 \text{ MVA} \quad \left(\begin{array}{l} \text{Rated power of the} \\ \text{transformer given on} \\ \text{the nameplate is an} \\ \text{output quantity} \end{array} \right)$$

$$P_{out} = 10 \times 0.8 = 8 \text{ MW}$$

$$I_2' = 10 \times 10^6 / 13.8 \times 10^3 = 725 \text{ A}$$
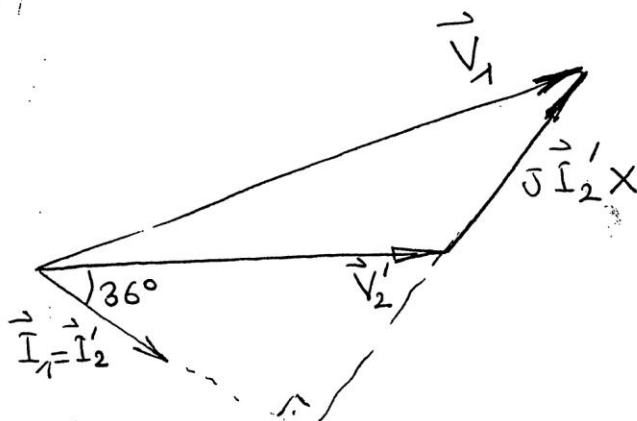
$$I_2 = 725 \times (13.8 / 79.7) = 125 \text{ A} \quad \left(I_2 < I_2' \text{ because it is a step-up transformer} \right)$$



phasor diagram

$$\vec{V}_1 = \vec{V}_2' + j\vec{I}_2' X$$

$$\vec{V}_1 = (13.8 + j0.0) \times 10^3 + j 1.9 \times 725 (0.8 - j0.6)$$

\uparrow reference phasor \uparrow $|I_2'|$ \uparrow 0.8 pf lagging
 $(\cos 36^\circ - j \sin 36^\circ)$

$$\vec{V}_1 = 13800 + j 1102 + 826.5$$

$$\vec{V}_1 = 14626.5 + j 1102$$

$$\vec{V}_1 = 14668 \angle 4.3^\circ$$


$$|\vec{V}_1| = 14.7 \text{ kV}$$

$$\begin{aligned} \text{Reg} &= \frac{V_1 - V_2'}{V_2'} \times 100 \\ &= \frac{14.7 - 13.8}{13.8} \times 100 \\ &= +6.5 \% \end{aligned}$$

Now solve the same problem for the leading load

$$\vec{V}_1 = 13.8 \times 10^3 + j 1.9 \times 725 (0.8 + j0.6)$$

\uparrow leading pf

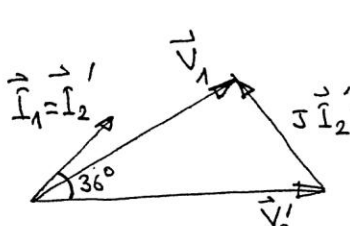

$$|\vec{V}_1| = 13 \text{ kV}$$

\uparrow less than 13.8 kV because of the ~~leading~~ capacitive load

$$\text{Reg} = \frac{13 - 13.8}{13.8} \times 100 = -5.7 \%$$

\uparrow because of the capacitive load.