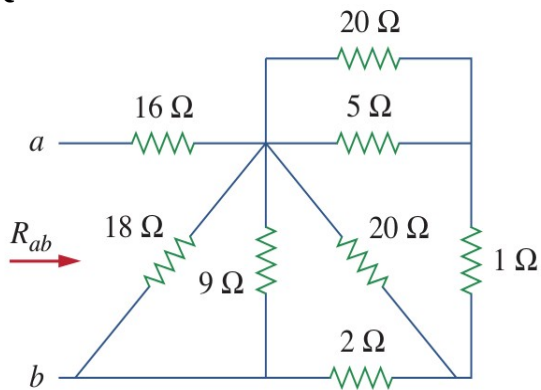


## EE281 – QUIZ #1 09/10/2014

Name:

Student No:

**Q-1 Find  $R_{ab}$  for the circuit below.**



**Q-2 In the circuit below, determine  $V_x$  and the power absorbed by the  $12\ \Omega$  resistor.**

