

Name:

ID:

EE 281 - Midterm Examination 1

November 3rd, 2014

1) a) Find the equivalent resistance between terminals *a* and *b*. (10 pts)

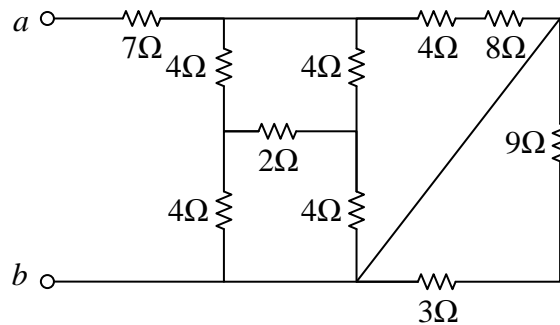


Fig 1.1

b) Find the equivalent resistance between terminals *a* and *b*. Note that the same resistor pattern goes to the infinity (10 pts)

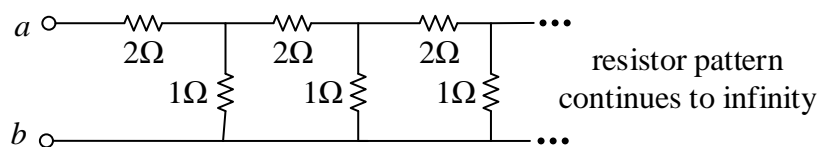


Fig 1.2

2) a) Write the node voltage equation for the essential node voltage, *e*, using only the given parameters. (10 pts)

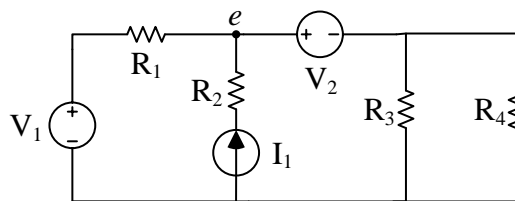


Fig. 2.1

b) Write the two mesh current equations necessary to analyze the given circuit, using only the given parameters. (10 pts)


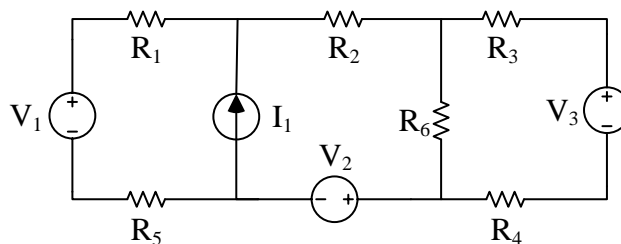


Fig. 2.2

3)

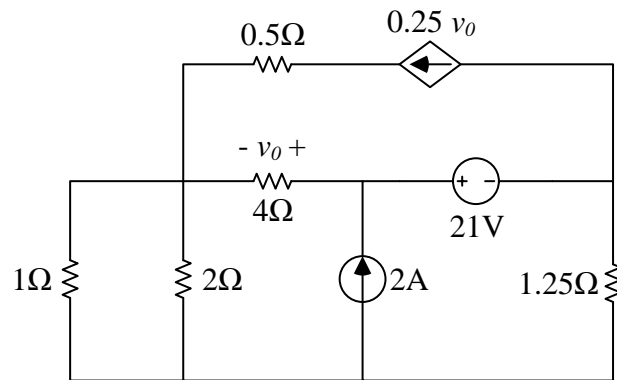

- Find v_0 using node voltage analysis method. (10 pts)
- Find v_0 using mesh current analysis method. (10 pts)
- Find the power absorbed/generated by each element. (10 pts)

4)

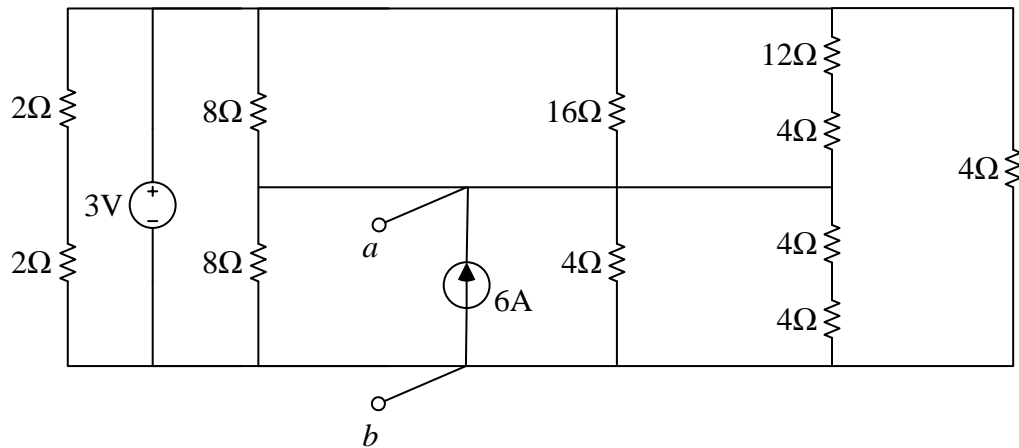


Fig. 4.1

- Consider the given circuit in Fig. 4.1. The circuit given in Fig 4.2 is the equivalent of the original circuit of Fig. 4.1. Find R_1 , R_2 and R_3 . (15 pts)

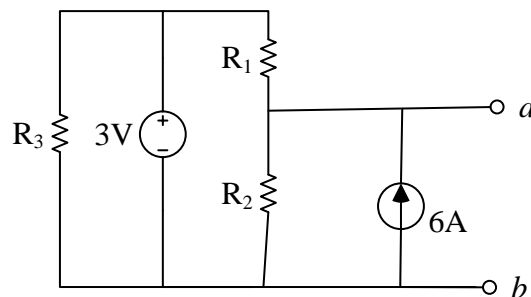


Fig. 4.2

- Find the Norton and Thevenin equivalents of the circuit given in Fig. 4.1, as seen between terminals a and b . Note that circuits of Fig. 4.1 and 4.2 are equivalent. (15 pts)