

Name:
ID:
Section:

EE 281 - Midterm Examination 2
December 8th, 2014

1) a) Find the Thevenin equivalent of the given circuit. (8 pts)

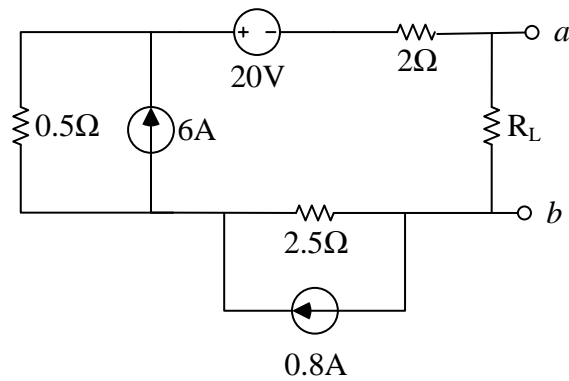


Fig 1.1

b) Connect a resistor between the terminals *a* and *b*, as seen in Fig 1.2. Find the power dissipated by R_L , for $R_L = 2.5\Omega$, $R_L = 5\Omega$, $R_L = 7.5\Omega$. (9 pts)

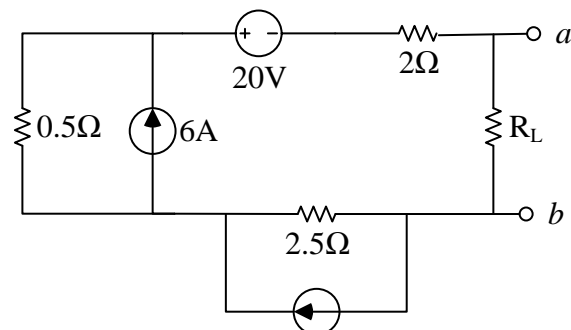


Fig 1.2

c) Comment on the results (3 pts)

2) a) Write the node voltage equation for the essential node voltages, v_1 and v_2 , using only the given parameters (represent v_0 in terms of v_1 and v_2). (10 pts)

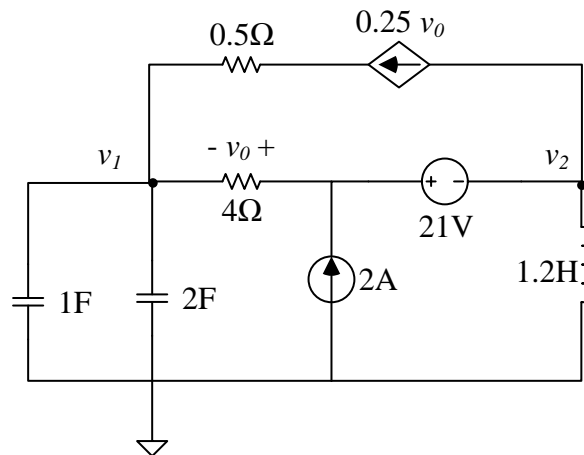


Fig. 2.1

b) Write the two mesh current equations necessary to analyze the given circuit, using only the given parameters. (10 pts)

3)

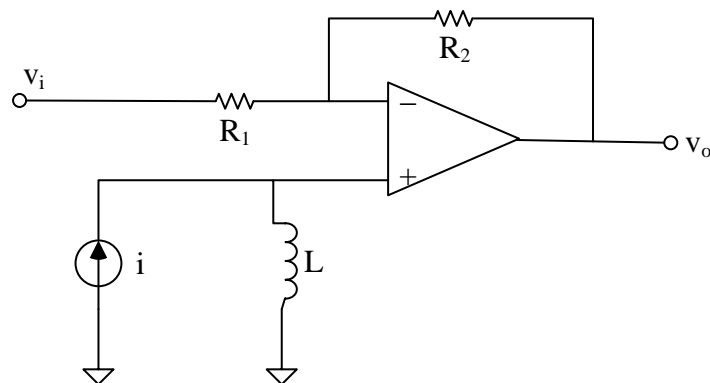


Fig. 3.1

a) Find v_0 in terms of v_i , R_1 , R_2 , i , L . (10 pts)

b) Assume;

$V_{ss} = 10V$ (Voltage at which the OpAmp goes into positive saturation region)

$V_{dd} = -10V$ (Voltage at which the OpAmp goes into negative saturation region)

$v_i = 5V$

$R_1 = 1k\Omega$

$R_2 = 3k\Omega$

$L = 0.5H$

$i = 0.1t^2$ (t is time in seconds)

Find the time instants at which;

- the OpAmp leaves the negative saturation region
- the OpAmp goes into the positive saturation region. (20 pts)

4) Consider the given circuits and voltage sources. Connect those components such that resulting output voltage will be;

$$v_0 = -10 \left(\int v_1(\tau) d\tau + v_2 + \frac{dv_3}{dt} \right)$$

Show all your work for full credit, including derivation of the input-output relations of the OpAmp circuits. (30 pts)

